

Electric Circuit symbols

Q1. Write the name for each of the circuit symbols in the box on the right

	
	
	
	
	
	
	
	
	
	
	
	
	
	